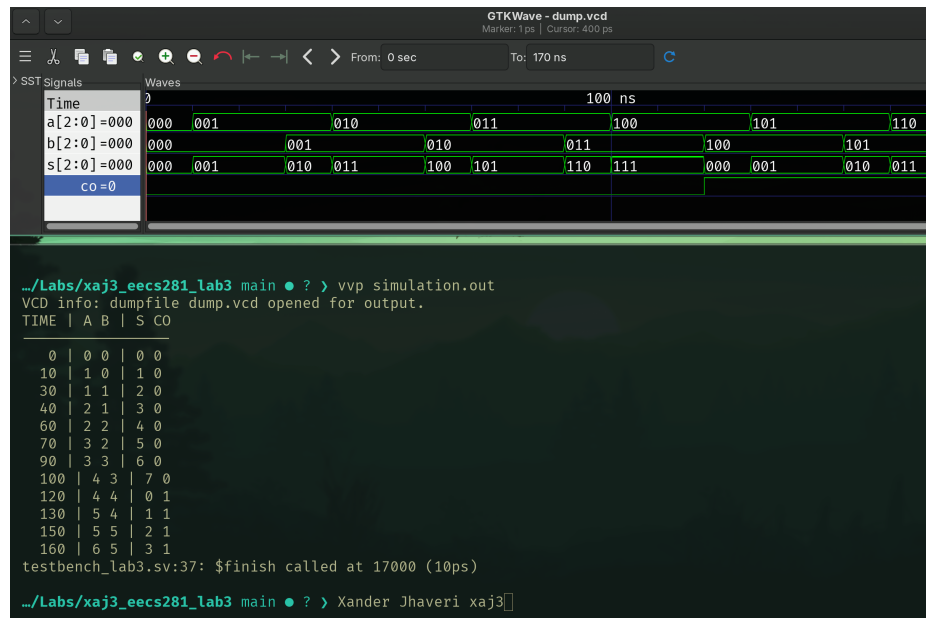


# Xander Jhaveri - Lab 3



Screenshot of the output from testbench\_lab3.sv

## rc\_adder\_slice.sv

```
module rc_adder_slice (
    input logic a,
    b,
    c_in,
    output logic s,
    c_out
);
    assign s = a ^ b ^ c_in;
    assign c_out = a & b | b & c_in | a & c_in;
endmodule
```

## rc\_adder4.sv

```
module rc_adder4 (
    input logic [2:0] a,
    input logic [2:0] b,
    output logic [2:0] s,
    output logic co
);
```

```

);

logic [3:0] c;
assign c[0] = 0;

rc_adder_slice adders[2:0] (
    .a(a),
    .b(b),
    .c_in(c[2:0]),
    .s(s),
    .c_out(c[3:1])
);

assign co = c[3];

endmodule

```

## testbench\_lab3.sv

```

`timescale 1ns / 10ps

module testbench_lab3 ();

    logic [2:0] a, b, s;
    logic co;

    rc_adder4 UUT (
        .a (a),
        .b (b),
        .s (s),
        .co(co)
    );

    initial begin
        a = 0;
        b = 0;
        forever begin
            #10 a++;
            #20 b++;
        end
    end

    initial begin
        // The following 2 lines output the file as a waveform
        // because I didn't use Model Sim
        $dumpfile("dump.vcd");
        $dumpvars(0, testbench_lab3);
    end

```

```
$display("TIME | A B | S CO");  
$display("_____");  
$monitor("  %2d | %d %d | %d %b", $time, a, b, s, co);  
  
#170;  
$finish();  
end  
  
endmodule
```